Project Description:

This project uses an **Arduino Uno**, **8 pushbuttons**, and a **piezo buzzer** to create a simple piano. Each button is assigned a different frequency, producing a distinct musical note when pressed.

Components Used:

- Arduino Uno
- 8 Pushbuttons (connected to digital pins 2 to 9)
- Piezo Buzzer (connected to pin 13)
- **Resistors** (if needed) for pull-downs or using internal pull-ups

How It Works:

- Each **pushbutton** is connected to a digital pin.
- When a button is **pressed**, the corresponding frequency is played on the **buzzer** using the tone() function.
- The tone (pin, frequency, duration) function generates the sound with a specific frequency and duration.
- A small delay prevents button press misreads.